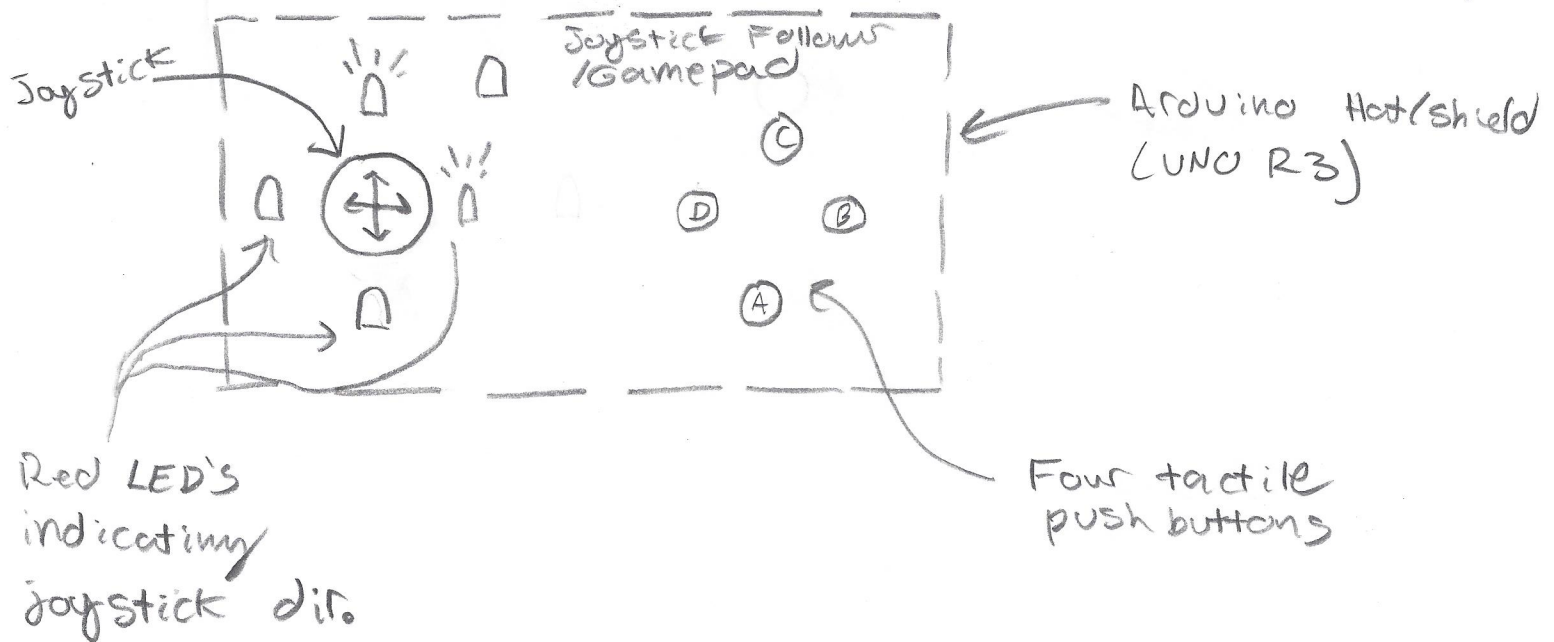


JoyStick Follower

Operation:

- A 2 axis Joystick (POT based) is read through the analog pins of the Arduino (A0, A1)
- The joystick has a pushable button that is read through a digital input pin
 - Pull-up / Pull-Down ?
- 4 LEDs are used to indicate the direction the joystick is pointing
- 1 LED activates when pushbutton is held down
- Add four additional buttons for other user inputs (digital inputs as well).
- The PCB should be an Arduino Hat for UNO R3.



- Recall, a Joystick is 2 potentiometers

Rough Schematic

